

Introduction to Electronics



An introduction to electronic components and a study of circuits containing such devices.

Week 1: Review





Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Circuit Elements

Review linear circuit components and properties




Lesson Objectives


⦿ Review

- Resistors, capacitors, inductors
 - i-v characteristics of these elements
- Sources, nodes


Passive Elements

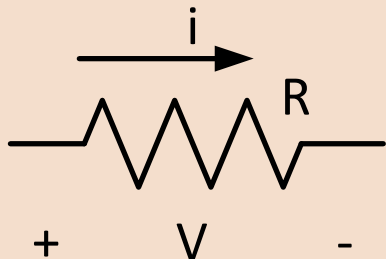Resistor

$$V = iR$$

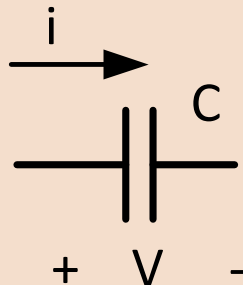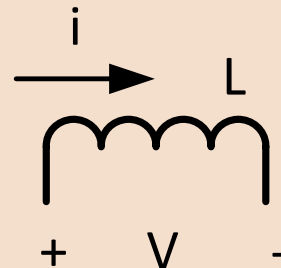
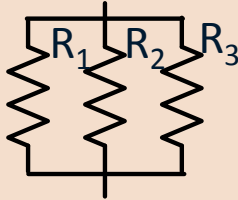

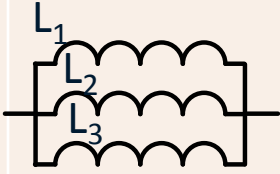
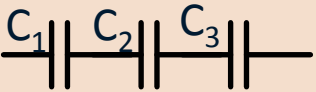
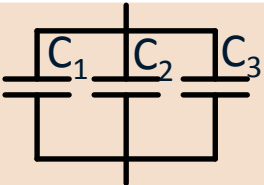
Capacitor

$$i = C \frac{dV}{dt}$$







Inductor

$$V = L \frac{di}{dt}$$



Series and Parallel Connections

	Series	Parallel
Resistors	 $R = R_1 + R_2$	 $R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$
Inductors	 $L = L_1 + L_2$	 $L = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$
Capacitors	 $C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$	 $C = C_1 + C_2 + C_3$

Connections and Sources

Ground		Reference for 0 volts
Node		Voltage level the same everywhere on the node
Voltage Source	Independent 	Dependent 
Current Source	Independent 	Dependent 

Circuit Connections

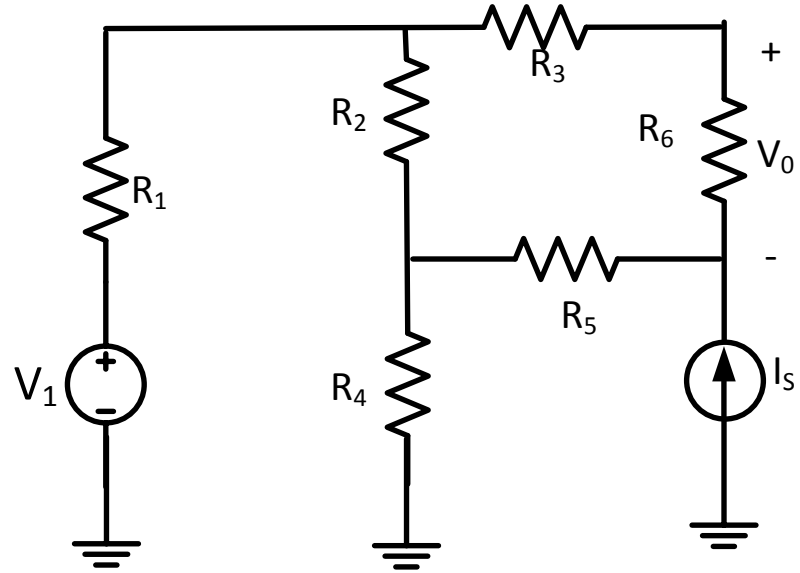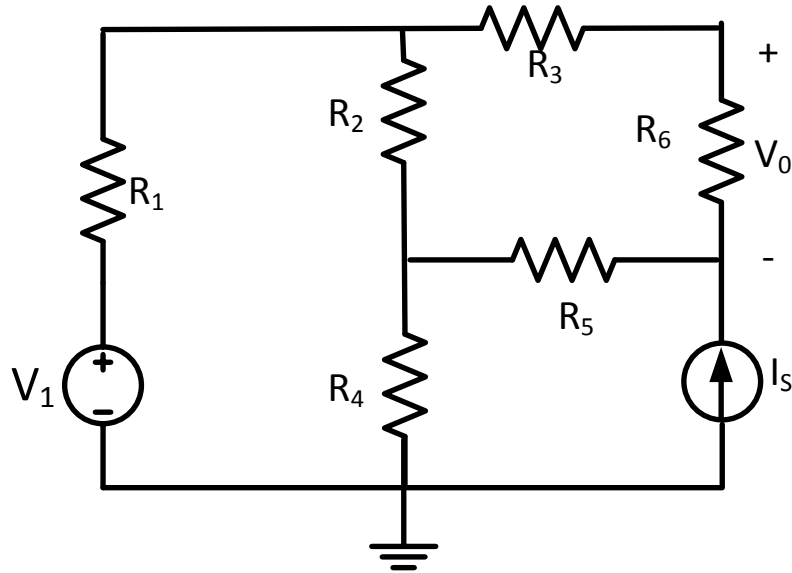



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Kirchoff's Laws

Review of KVL and KCL




Lesson Objectives

◉ Review


- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)

Kirchhoff's Voltage Law (KVL)

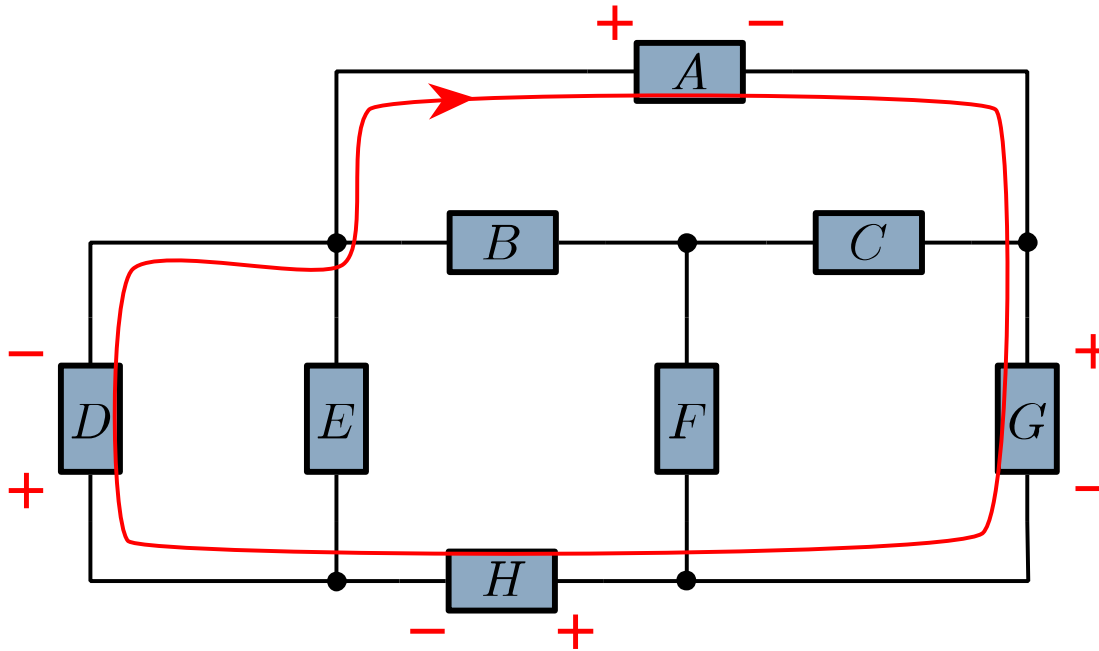


The sum of voltages around any closed loop is zero.

KVL Quiz

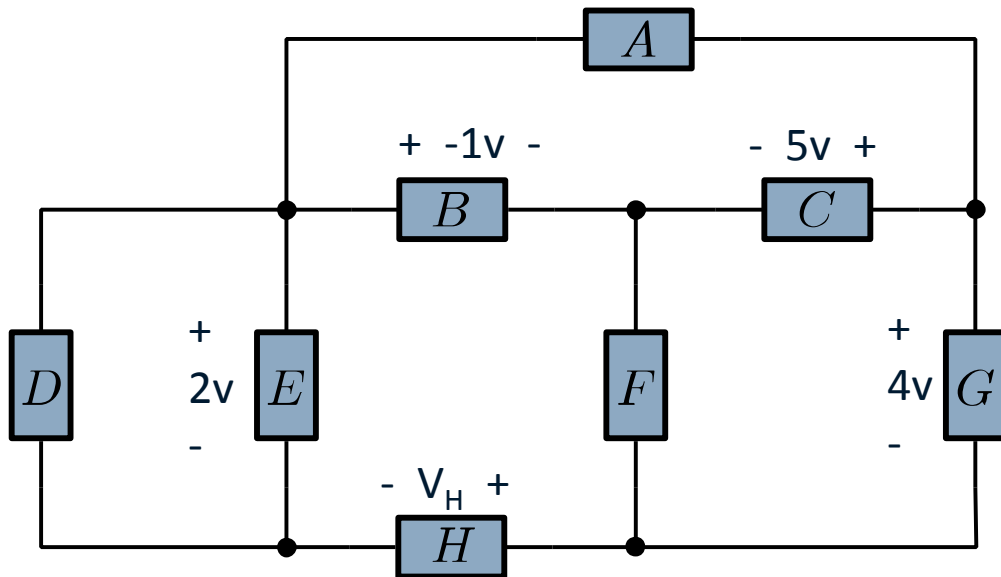


KVL and Parallel Circuits

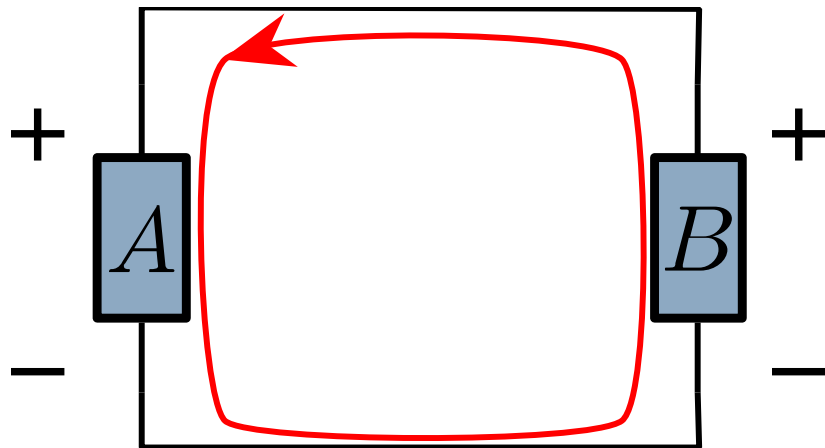


$$v_A - v_B = 0$$

$$v_A = v_B$$

KVL Example

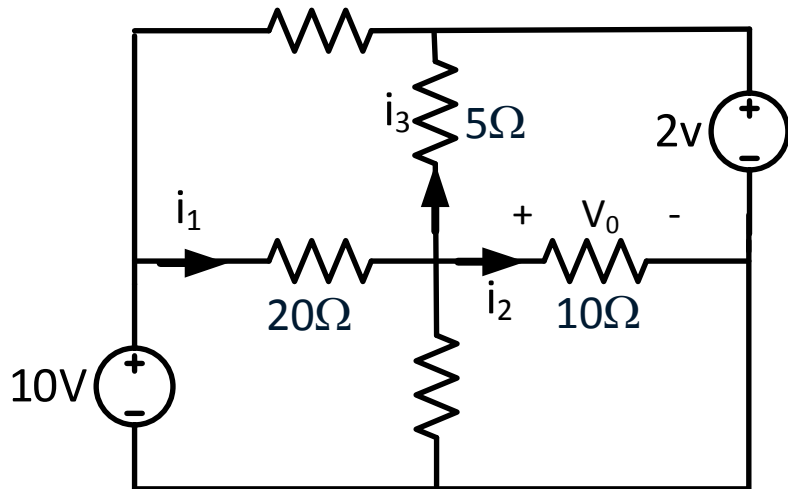


Kirchhoff's Current Law (KCL)

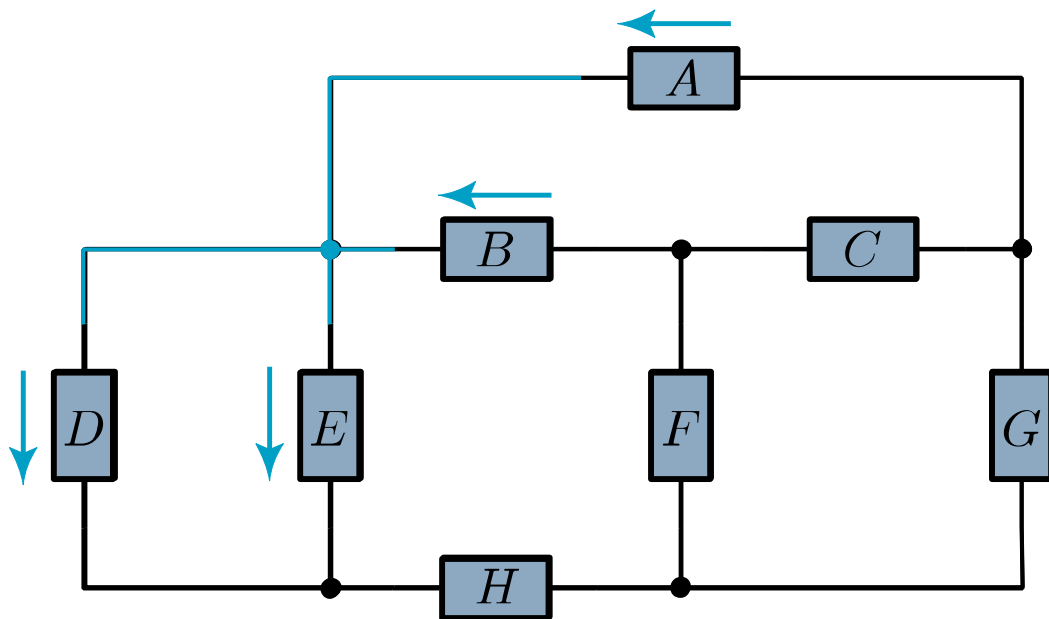


$$\sum i_{\text{entering}} = \sum i_{\text{leaving}}$$

KCL and Series Circuits

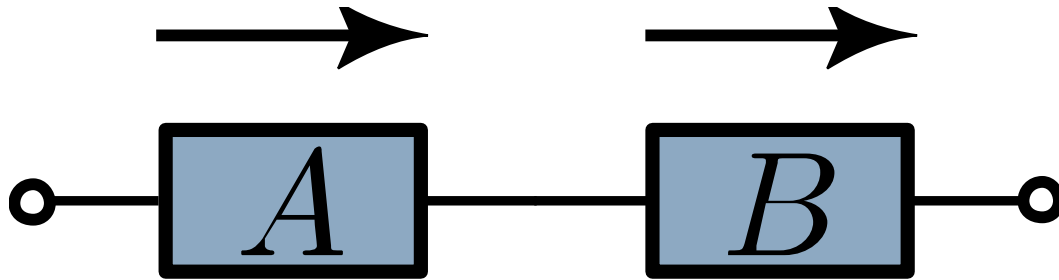

$$i_A = i_B$$

KCL Example

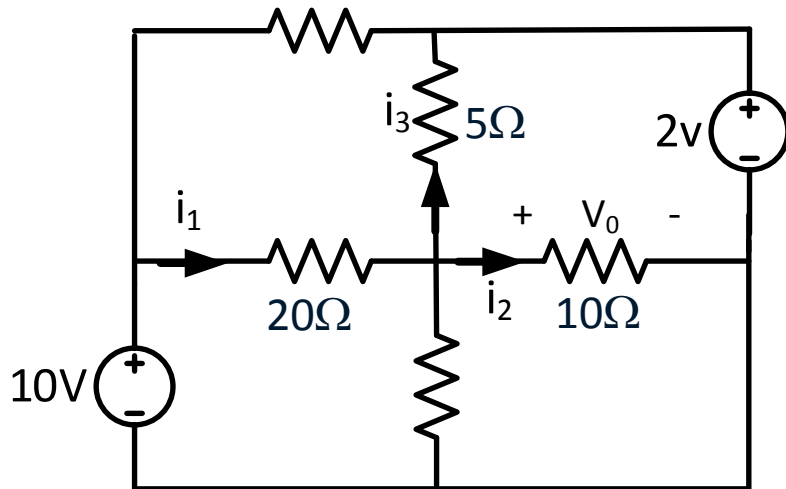

Summary

- Introduced KVL and KCL
- Applied KVL to parallel elements
- Applied KCL to series elements
- Solved a simple circuit using
Kirchhoff's Laws



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Impedance

Review of Impedance for Analyzing AC Circuits




Lesson Objectives

- Review
 - Impedances for steady-state sinusoidal inputs (AC)

Impedances

 R 

$$Z_R = R$$

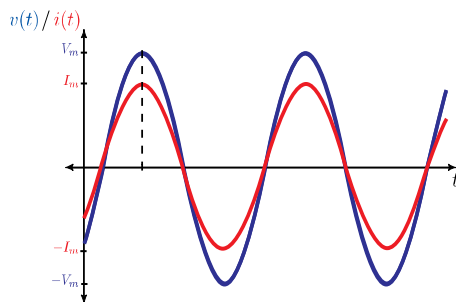


In-phase


Frequency invariant




$$Z_C = \frac{1}{j\omega C}$$

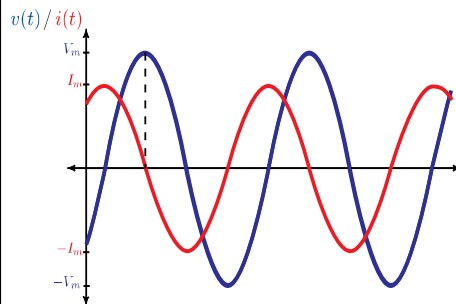

Current leads voltage

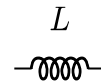


$$Z_L = j\omega L$$

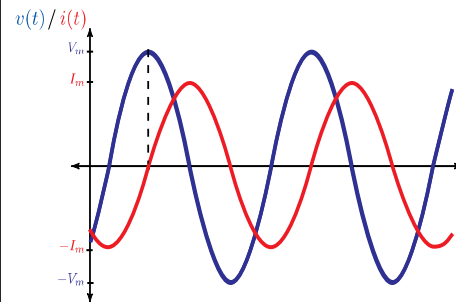


Current lags voltage

Impedances in Series

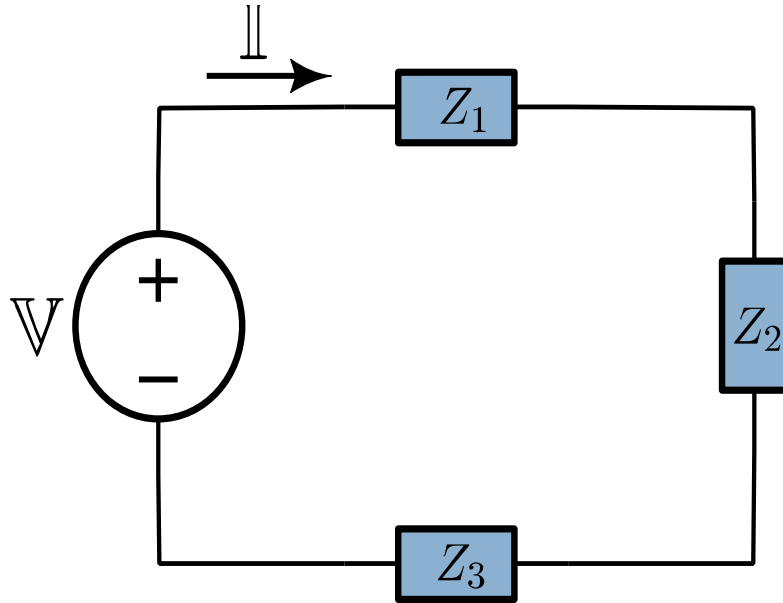

$$Z_{\text{cq}} = \sum_i Z_i$$


Impedances in Parallel

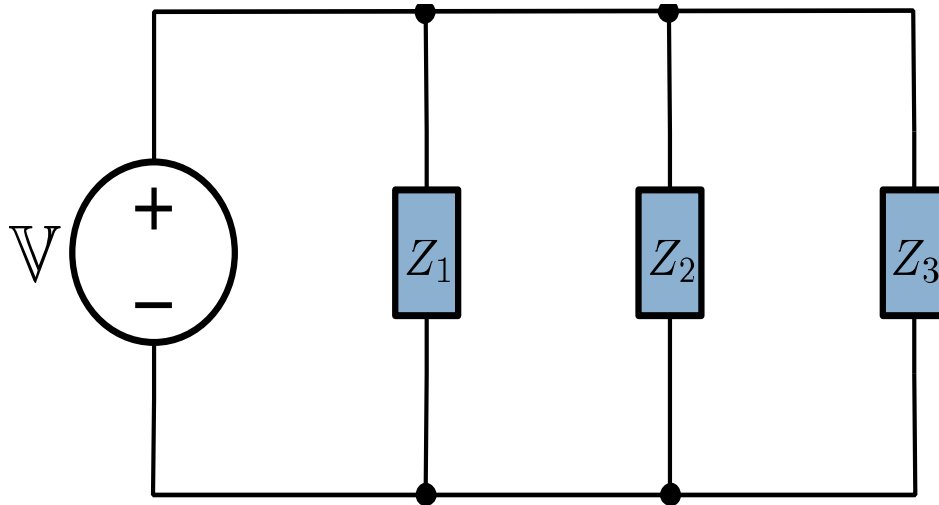


$$Z_{\text{eq}} = \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right]^{-1}$$

$$Z_{\text{eq}} = \left[\sum_i \frac{1}{Z_i} \right]^{-1}$$

Kirchhoff's Laws

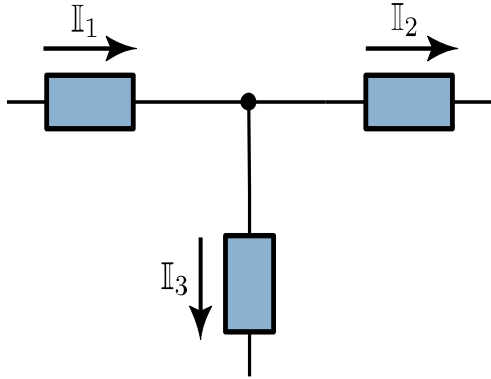


$$I_1 = I_2 + I_3$$

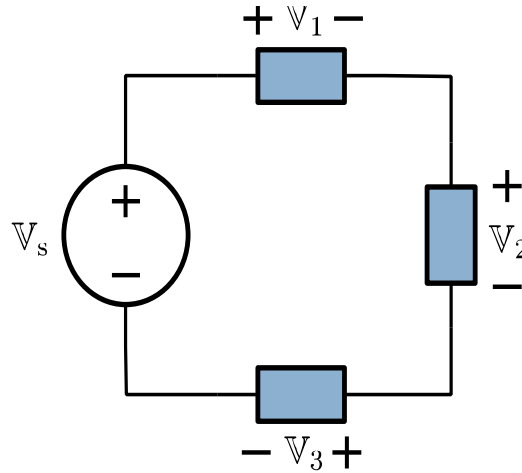


$$V_s = V_1 + V_2 + V_3$$

Series RC

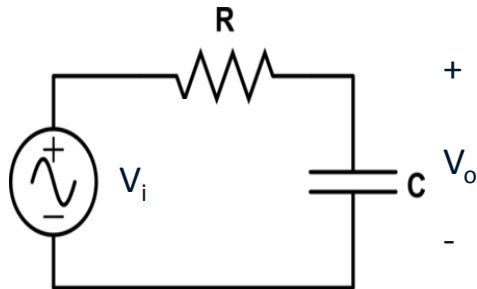

Series RLC

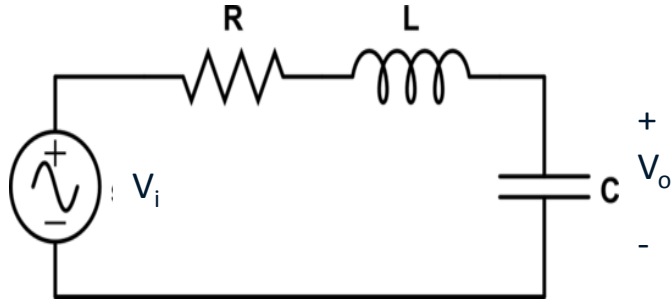

Summary

- Introduced KVL and KCL
- Applied KVL to parallel elements
- Applied KCL to series elements
- Solved a simple circuit using
Kirchhoff's Laws



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Transfer Functions


Review of transfer functions for characterizing circuits



Lesson Objectives

- Review transfer functions
 - To characterize a circuit
 - To find frequency response curves

Transfer Function Two-Port Networks



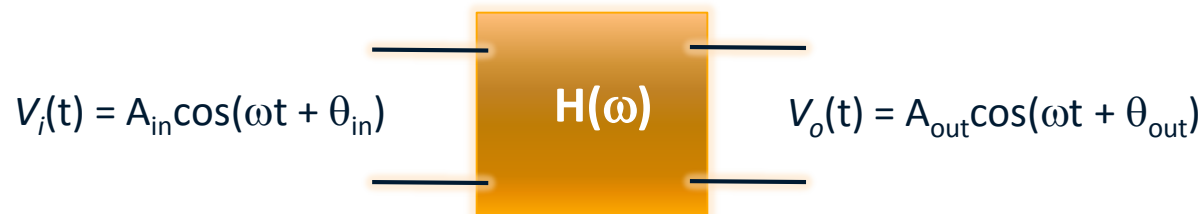


$$H(\omega)V_i = V_o$$

$$H(\omega)A_{in} \angle \theta_{in} = A_{out} \angle \theta_{out}$$

$$A_{out} = |H(\omega)|A_{in} \quad \theta_{out} = \angle H(\omega) + \theta_{in}$$

Summary of Simple Circuits

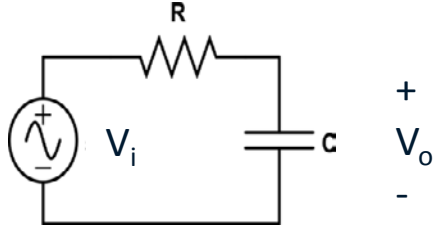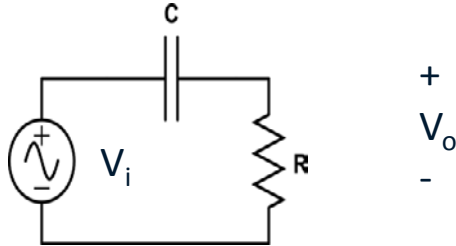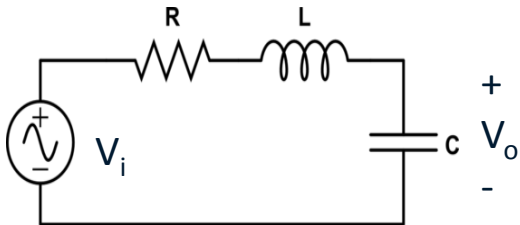	$H(\omega) = \frac{1}{1 + RC\omega j}$
	$H(\omega) = \frac{RC\omega j}{1 + RC\omega j}$
	$H(\omega) = \frac{1}{1 - \omega^2 LC + RC\omega j}$

Summary

- Defined transfer function for Two-Port Networks
 - Showed transfer functions of simple circuits



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Review of Frequency Response Plots (Bode)

*Review of linear plots and Bode plots to show the frequency
characteristics of signals and circuits*




Lesson Objectives

- Define the frequency response for a transfer function $H(\omega)$

Magnitude Plot: $|H(\omega)|$ vs ω
Angle Plot: $\angle H(\omega)$ vs ω

- Show linear plots and Bode plots

Frequency Response


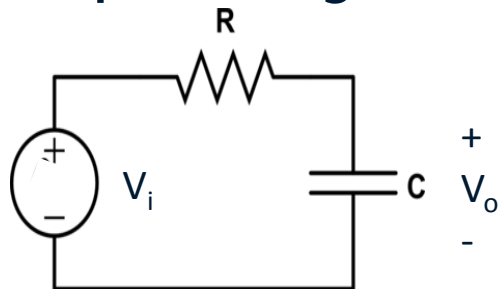


Transfer Function




$$H(\omega) = \frac{1}{1 + RC\omega j}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$
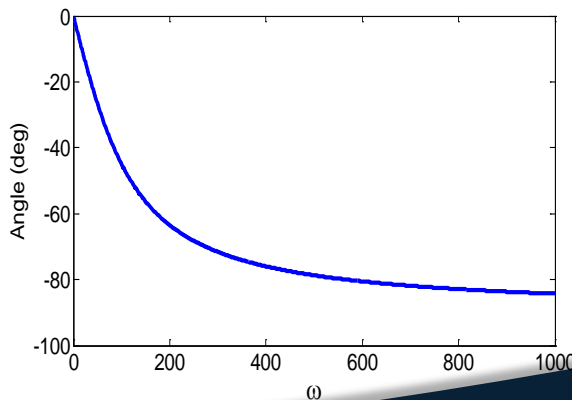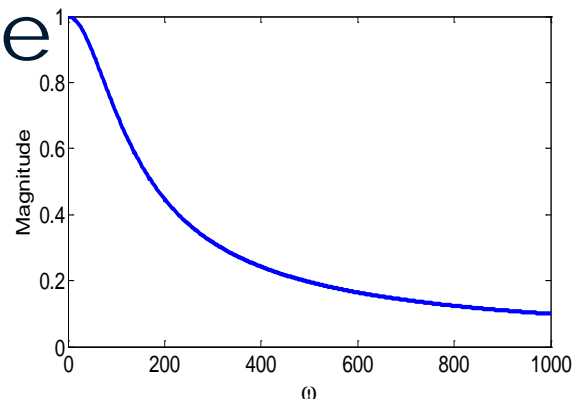
$$\angle H(\omega) = -\tan^{-1}(RC\omega)$$





Circuit Response

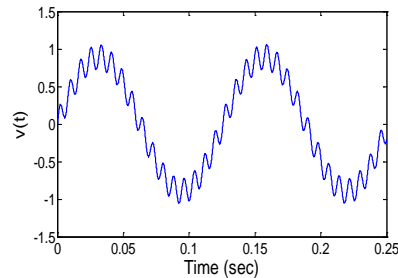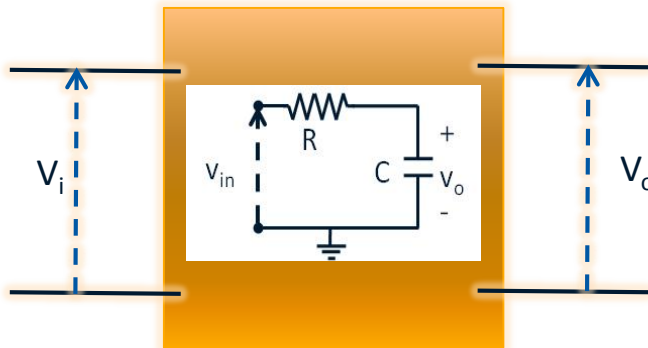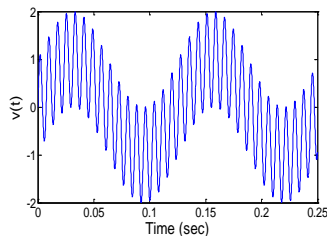


$$V_i = \cos(50t) + \cos(800t)$$



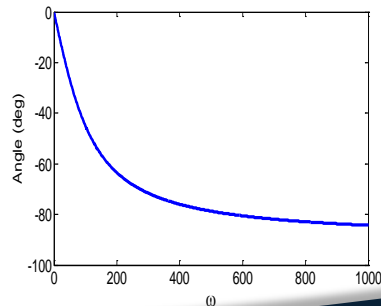
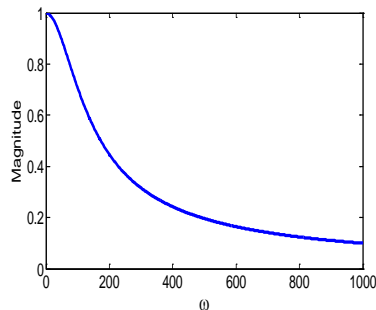
$$V_o = 0.95\cos(50t-20^\circ) + 0.13\cos(800t-85^\circ)$$




Bode Plots

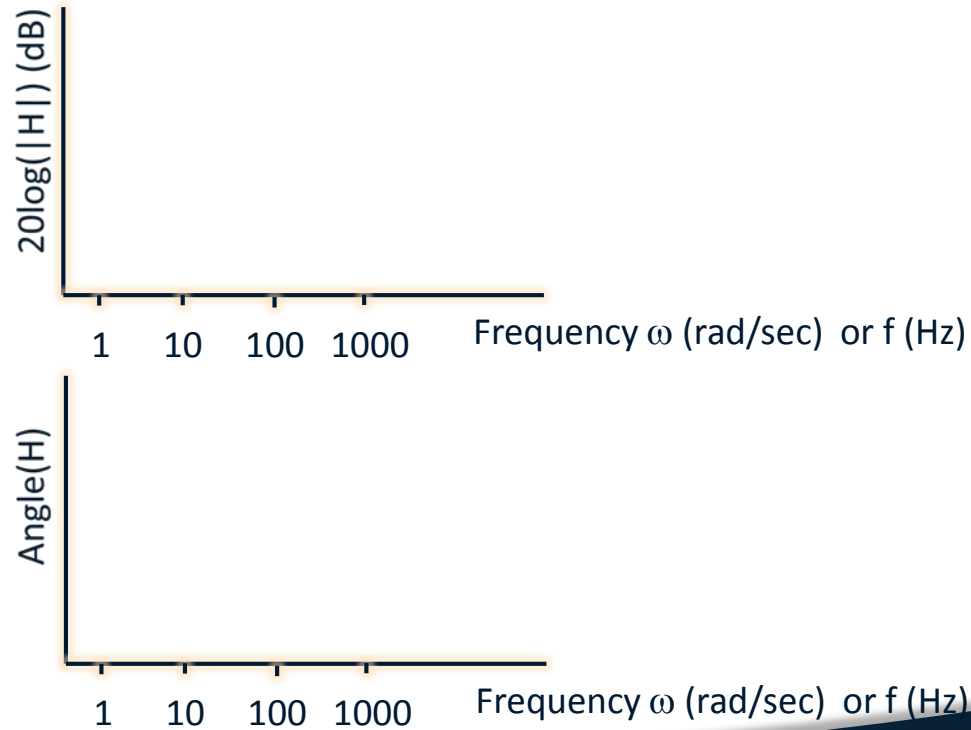

Linear Plot and Bode Plot

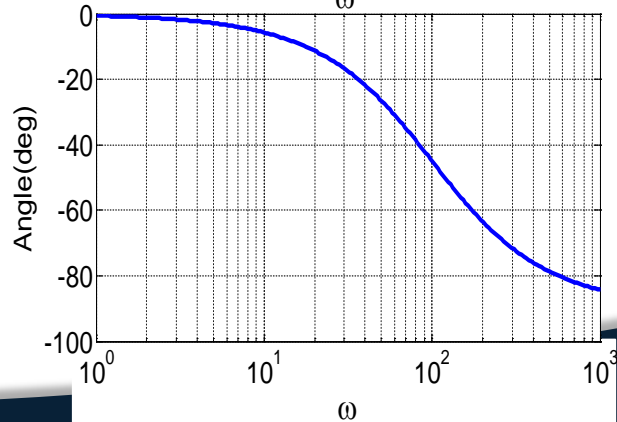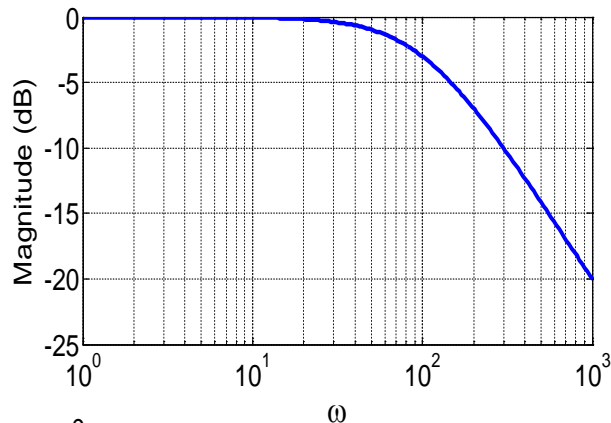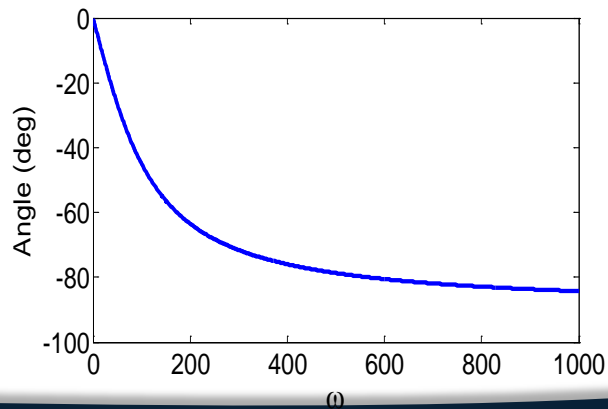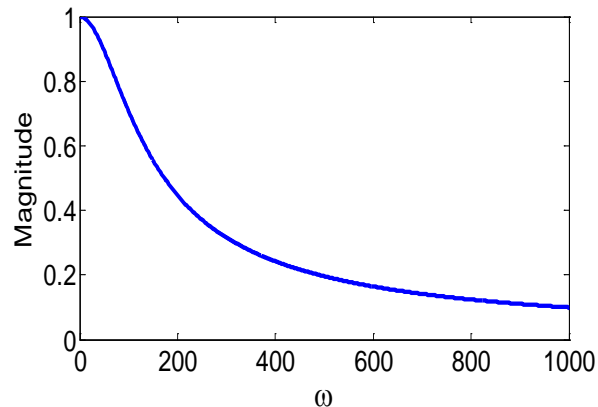

Bode Plot First-Order Characteristics


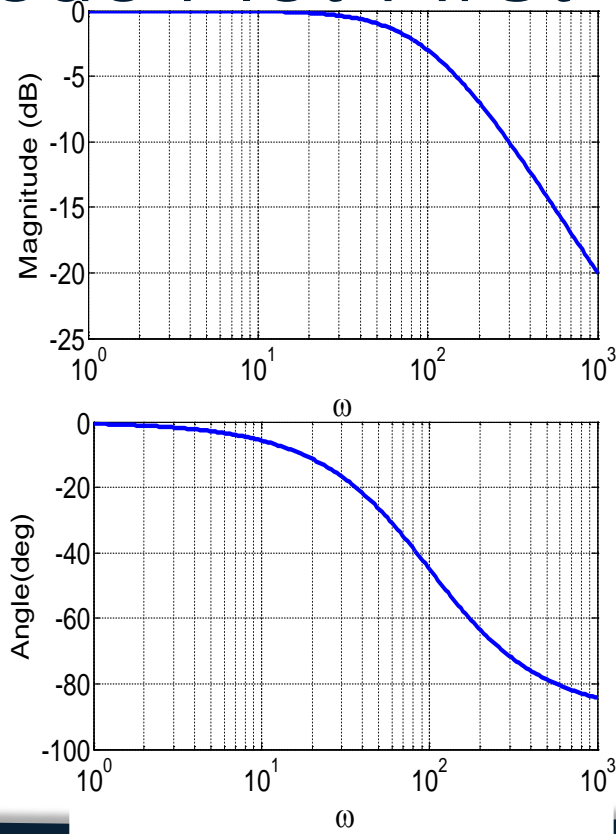


$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$


$$\angle H(\omega) = -a \tan(\omega RC)$$

Bode Plot of RLC Circuit, Overdamped

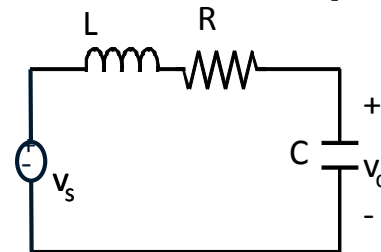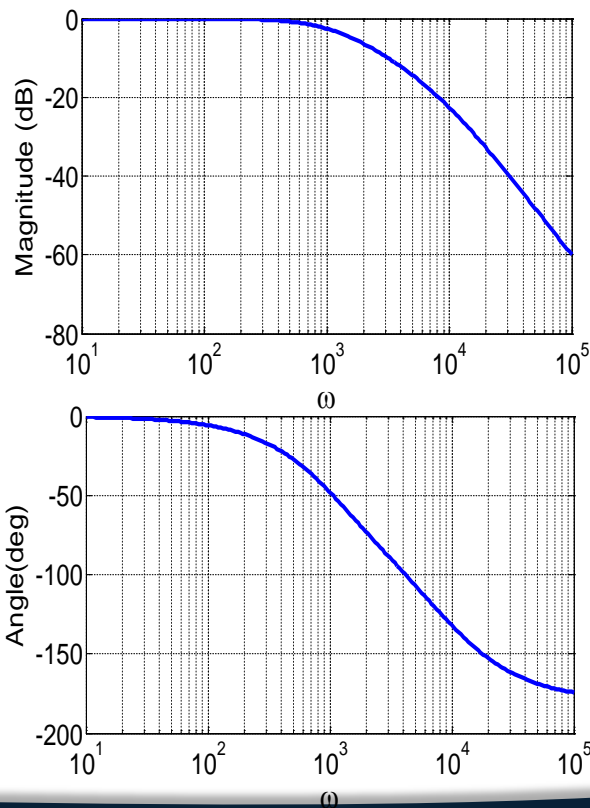

$$H(\omega) = \frac{1}{(1 - LC\omega^2) + RCj\omega}$$

Bode Plot of RLC Circuit, Underdamped

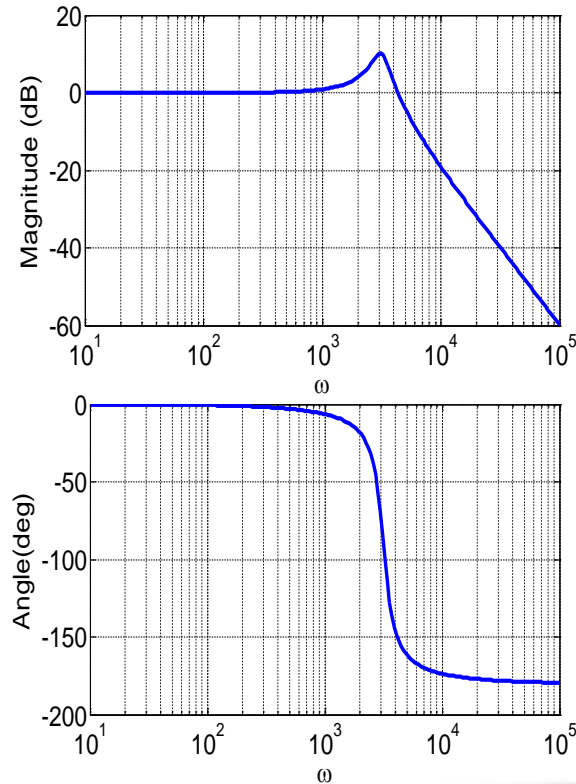

Summary

- A **frequency response** is a plot of the transfer function versus frequency
- The frequency response can be used to determine the steady-state sinusoidal response of a circuit at different frequencies