

# Introduction to Electronics



*An introduction to electronic components and a study of circuits containing such devices.*

# Week 6: MOSFETs





**Dr. Bonnie Ferri**

Professor and Associate Chair  
School of Electrical and  
Computer Engineering

# Introduction and MOSFET Physics

*Study the physics of MOSFETs*



# Lesson Objective

- Introduce the uses of transistors
- Investigate the physics of MOSFETs


# Types of Transistors

- MOSFET (metal-oxide-semiconductor silicon field-effect transistor)
- BJT (bipolar junction transistor)


# Uses of Transistors

- ⦿ Electrically controlled switch (digital circuits/computers)
- ⦿ Amplifier (op amps)
- ⦿ Resistor with value electrically controlled


# NMOS (N-type MOSFET)

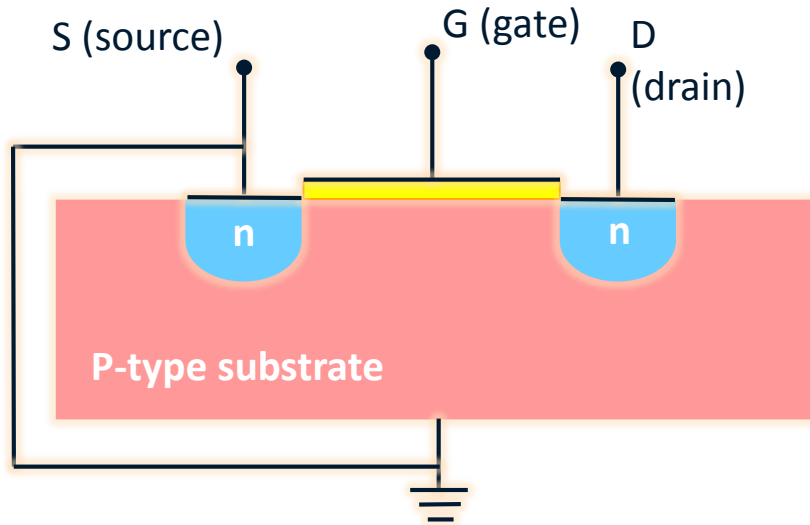

# NMOS: Vary $V_G$

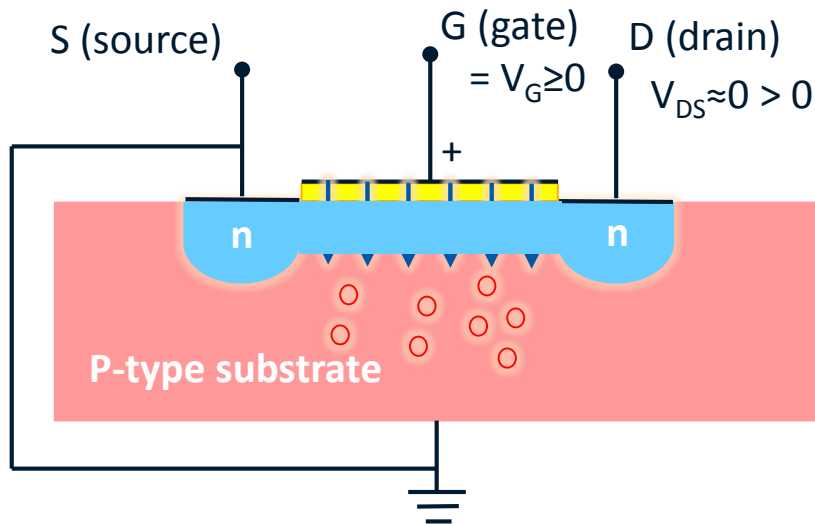


$V_{DS}$  small and constant

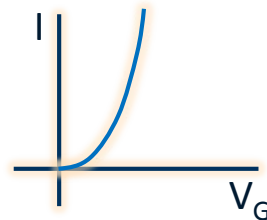





# NMOS: Vary $V_{DS}$

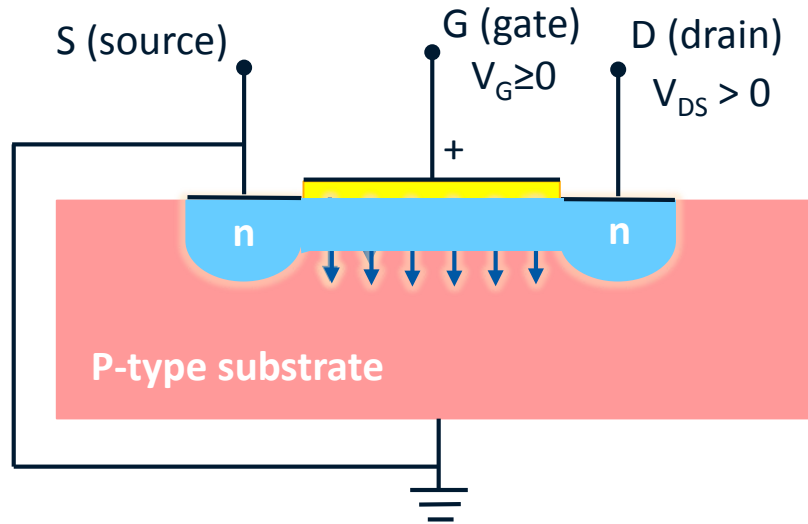

$V_G$  constant

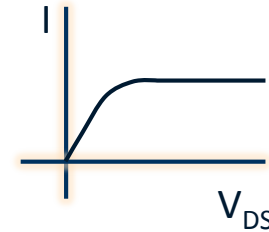

# Summary

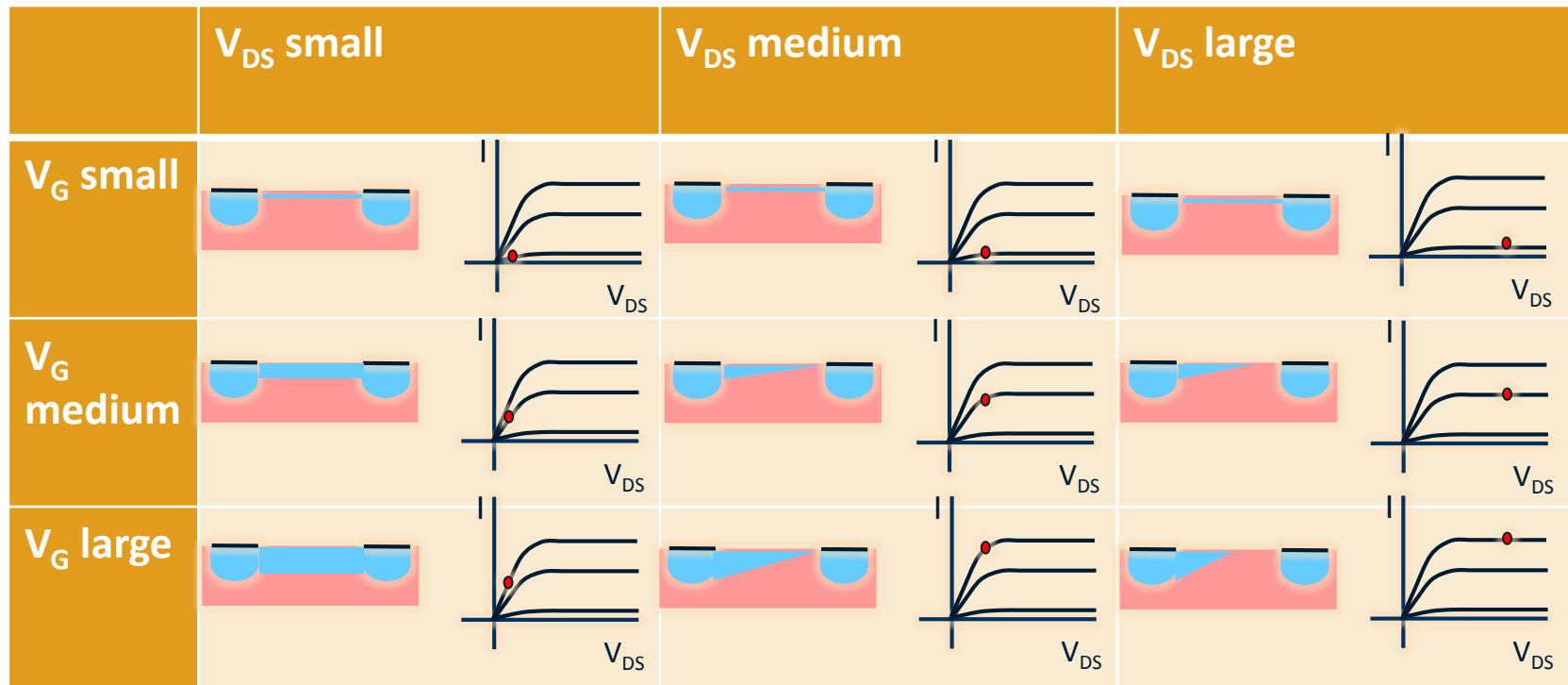

# Remainder of Module

- ⦿ MOSFET switches
- ⦿ MOSFET amplifiers
- ⦿ BJTs

# MOSFET Switches



**Dr. Bonnie Ferri**

Professor and Associate Chair  
School of Electrical and  
Computer Engineering

*Introduce the use of MOSFETs as switches in circuits*




# Previous Lesson

- Introduction to MOSFETs
- The physics of MOSFETs


# Lesson Objectives

- Examine the use of MOSFET as a switch in a circuit
- Introduce CMOS devices

# NMOS Switch Behavior

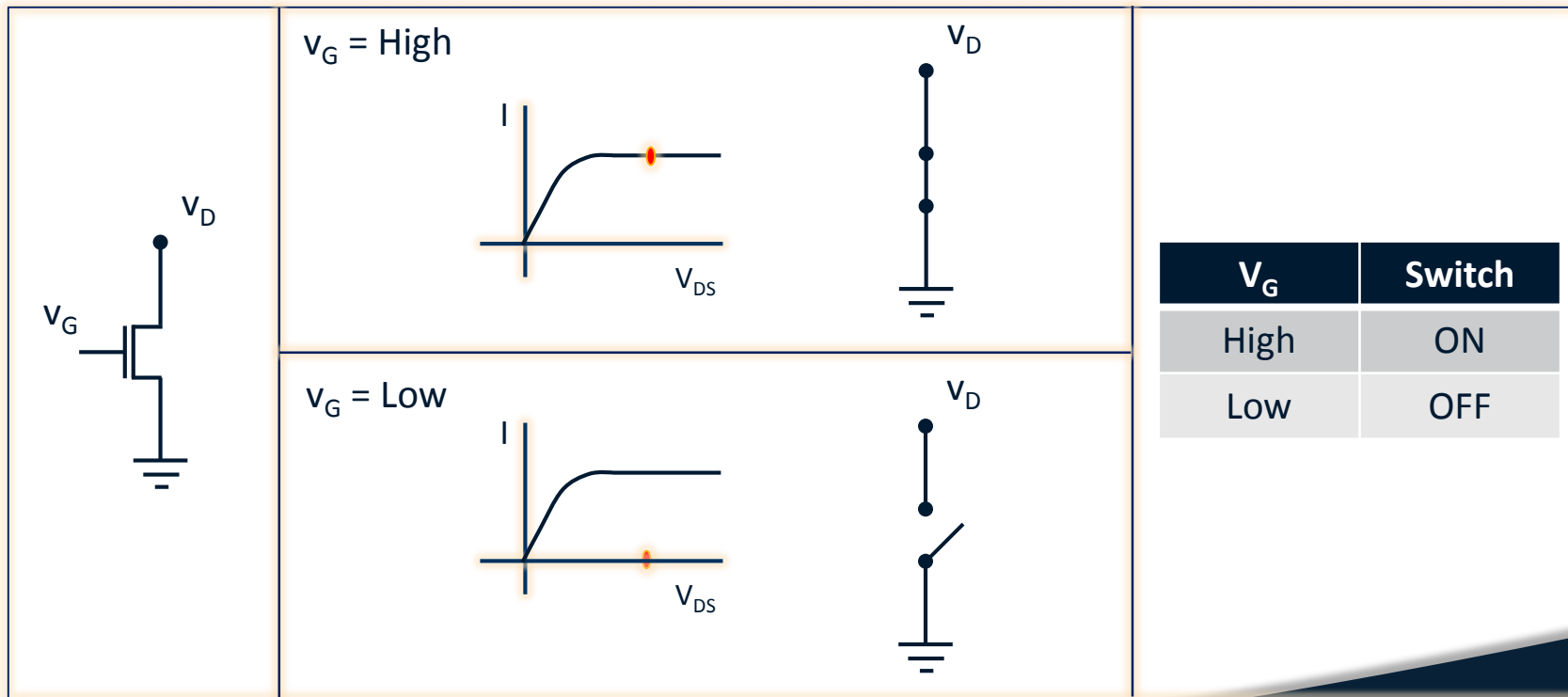


# Simple NMOS Inverter Circuit

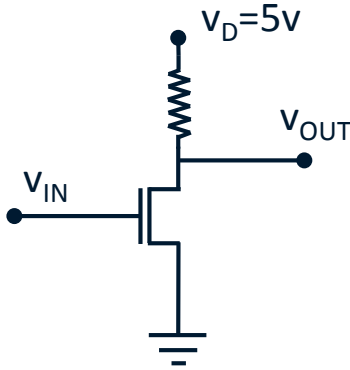



# CMOS Devices

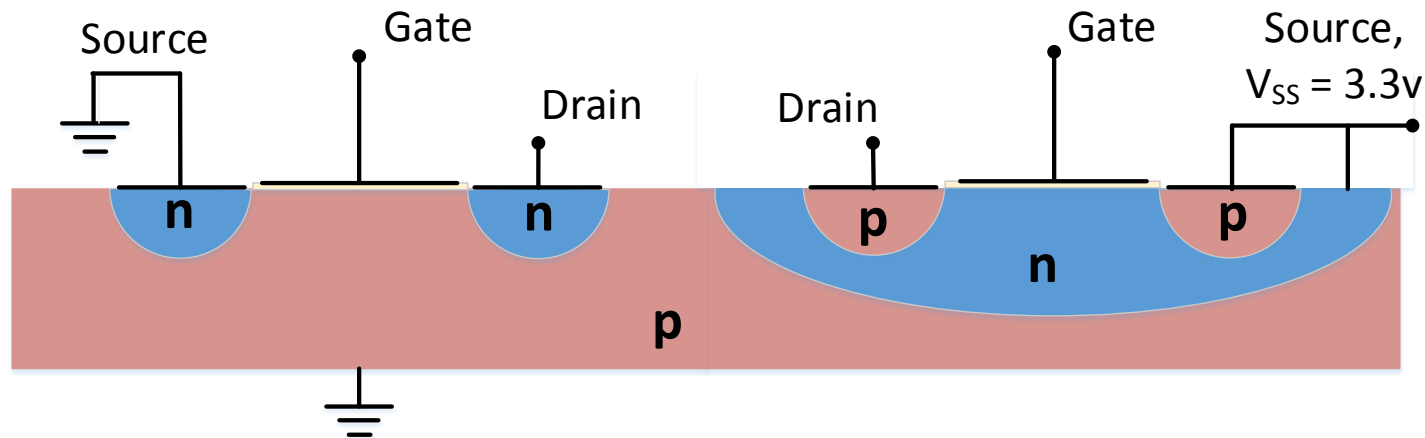

**NMOS:**


$V_G$	Switch
High	ON
Low	OFF

**PMOS:**

$V_G$	Switch
High	OFF
Low	ON

# Summary of Switch Behavior

## NMOS

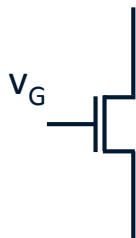


$V_G$	Switch
High	ON
Low	OFF

## PMOS



$V_G$	Switch
High	OFF
Low	ON

# CMOS Inverter Circuit

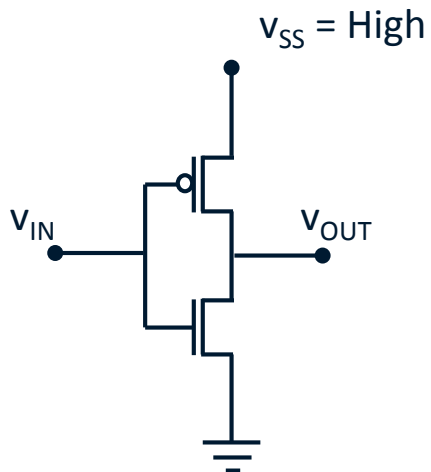

$V_{IN}$	$V_{OUT}$
High	Low
Low	High

# Summary

- Examine the use of MOSFET as an electrically controlled switch in a circuit
- Introduced CMOS for complementary p-type and n-type transistor behavior
- Introduced inverter circuits

# CMOS Logic Gates



**Dr. Bonnie Ferri**

Professor and Associate Chair  
School of Electrical and  
Computer Engineering

*Introduction to logic gates made from CMOS transistors*






# Previous Lesson

## ○ MOSFET Switches

# Lesson Objectives

- Introduce logic gates and their transistor circuits
  - NOT, NAND, NOR, AND, OR

# CMOS NOT Gate (Inverter Circuit)

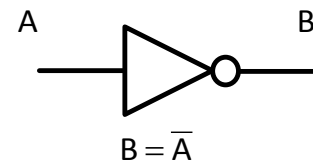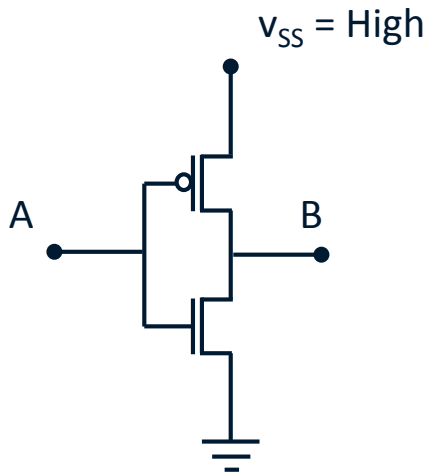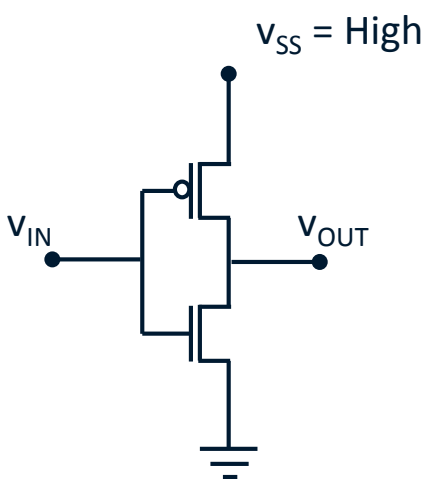

**Truth Table**

$V_{IN}$	$V_{OUT}$
High	Low
Low	High


A	B
0	1
1	0



# Logic Gates


## NOT

A	B
0	1
1	0

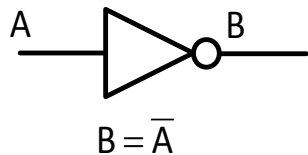


## AND

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

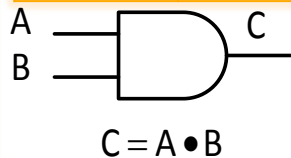


## NAND

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

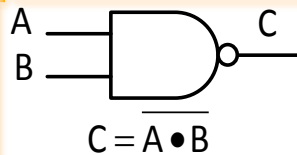


## OR

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

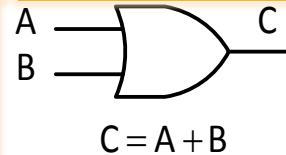


## NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

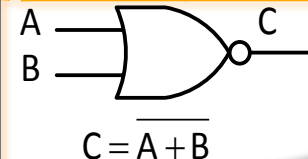


# PMOS Switch Behavior

## NMOS

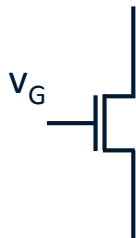

$V_G$	Switch
High	ON
Low	OFF

## PMOS



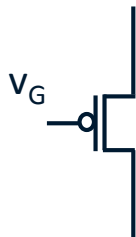


$V_G$	Switch
High	OFF
Low	ON

# NAND Gate

## NAND




A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

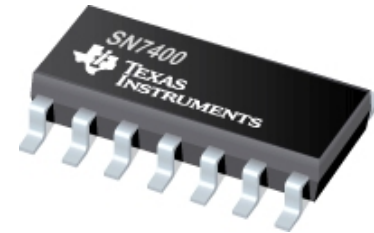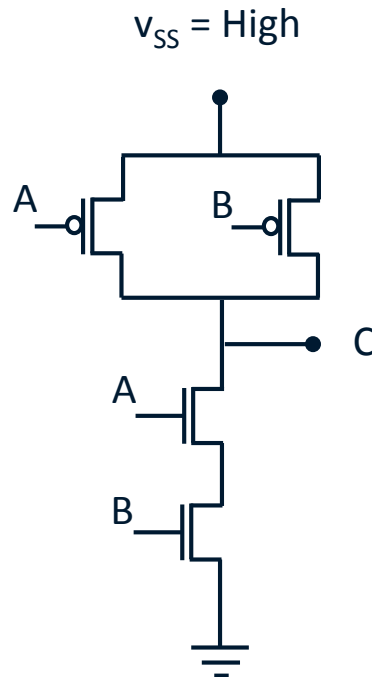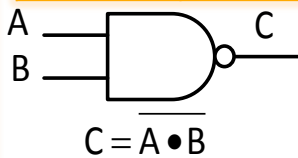

# NOR Gate

## NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

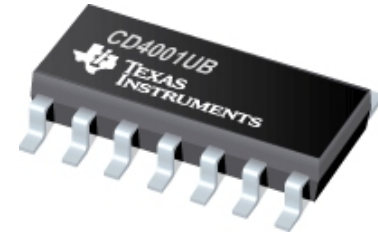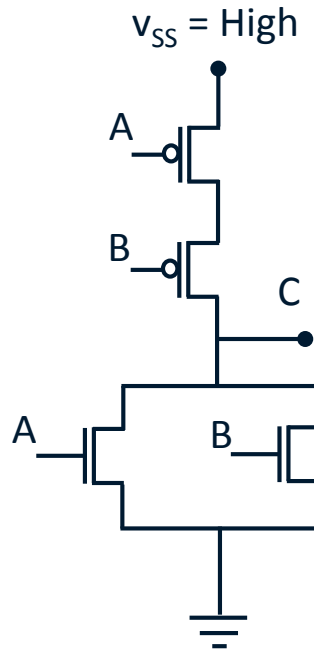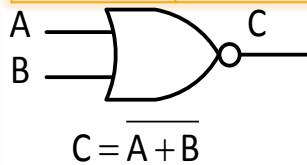

# Summary


- Logic gate circuits are made from CMOS n-type and p-type transistors



**Dr. Allen Robinson**

Academic Professional  
School of Electrical and  
Computer Engineering

# Introduction to Electronics



*An introduction to electronic components and a study of circuits  
containing such devices.*



**Dr. Allen Robinson**  
Academic Professional  
School of Electrical and  
Computer Engineering

# MOSFET Characteristics

*Introduce MOSFET characteristic curves and biasing*



# Previous Lesson

- Introduced CMOS logic gates




# Lesson Objectives


- Introduce MOSFET characteristic curves
- Introduce dc biasing

# Characteristic Curves

MOSFET Output Characteristics

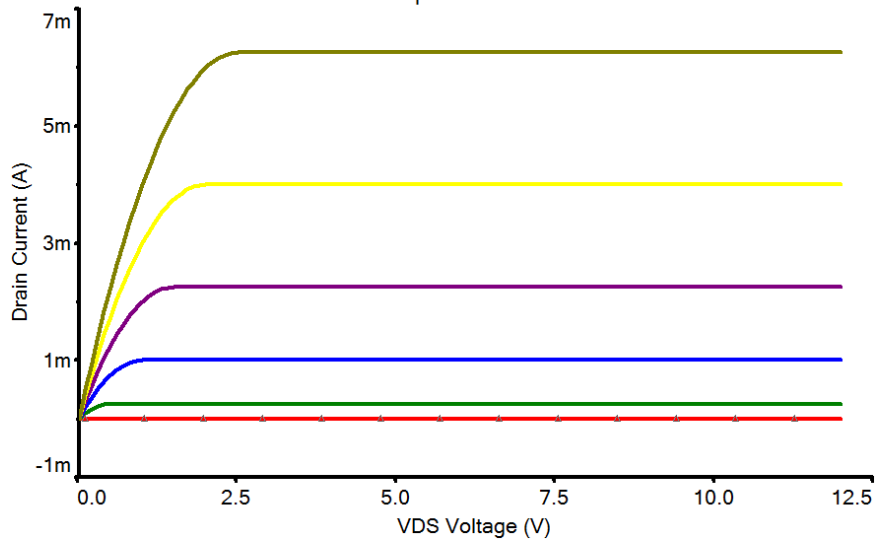


MOSFET Transfer Characteristic

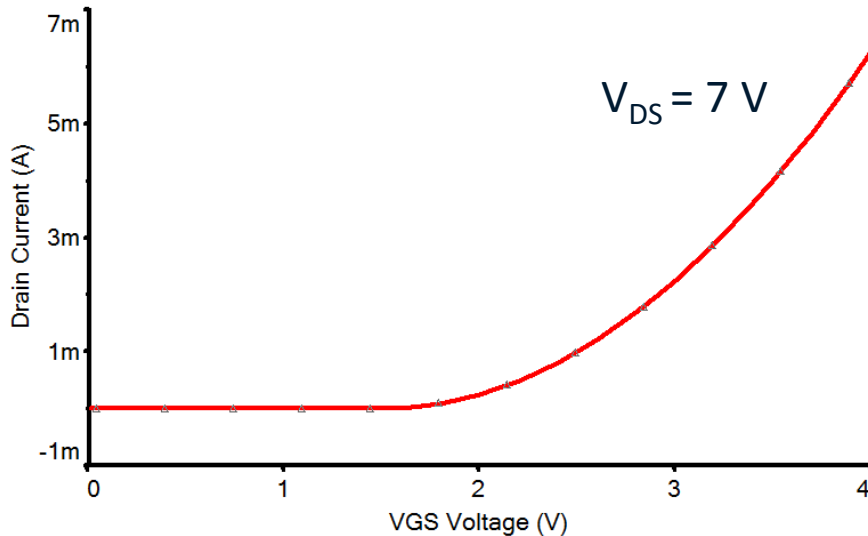

# Regions of Operation

MOSFET Output Characteristics

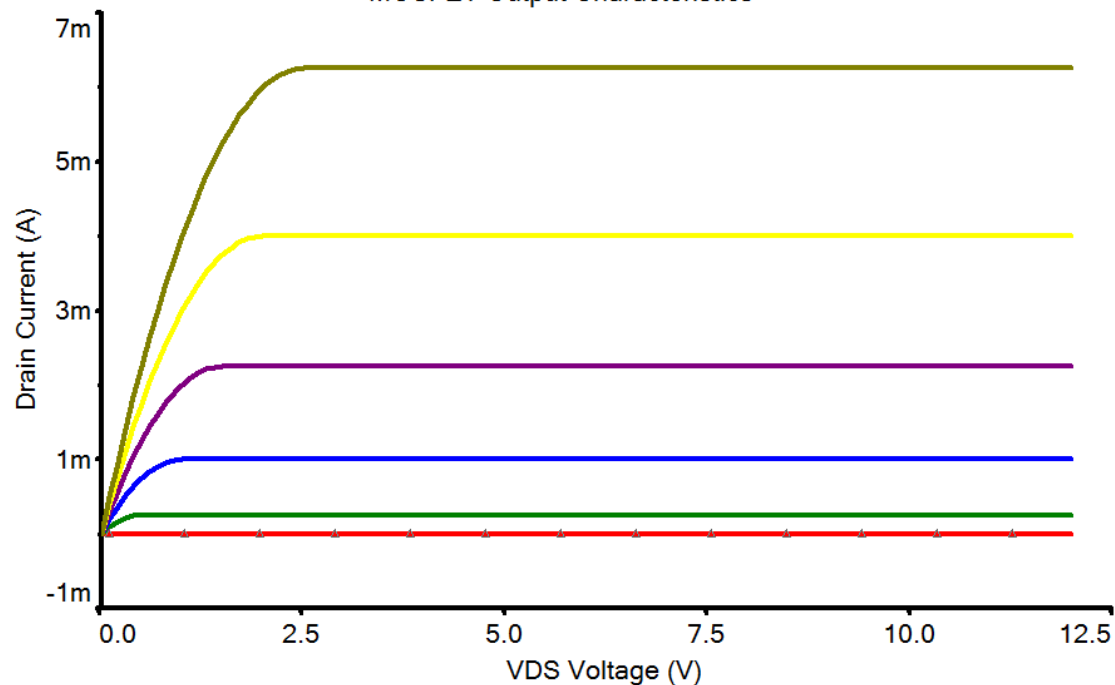

# Regions of Operation

Cutoff Region

$$V_{GS} < V_{TO}$$

$$I_D = 0$$

Linear/Triode Region

$$V_{GS} > V_{TO}$$

$$V_{DS} < V_{GS} - V_{TO}$$

$$I_D = 2K \left[ (V_{GS} - V_{TO}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Saturation Region

$$V_{GS} > V_{TO}$$


$$V_{DS} > V_{GS} - V_{TO}$$

$$I_D = K(V_{GS} - V_{TO})^2$$

$K$  = Transconductance parameter. Units of  $A/V^2$

$V_{TO}$  = Threshold or turn on voltage. Minimum value of  $V_{GS}$  for  $I_D$  to flow.

# Transfer Characteristics

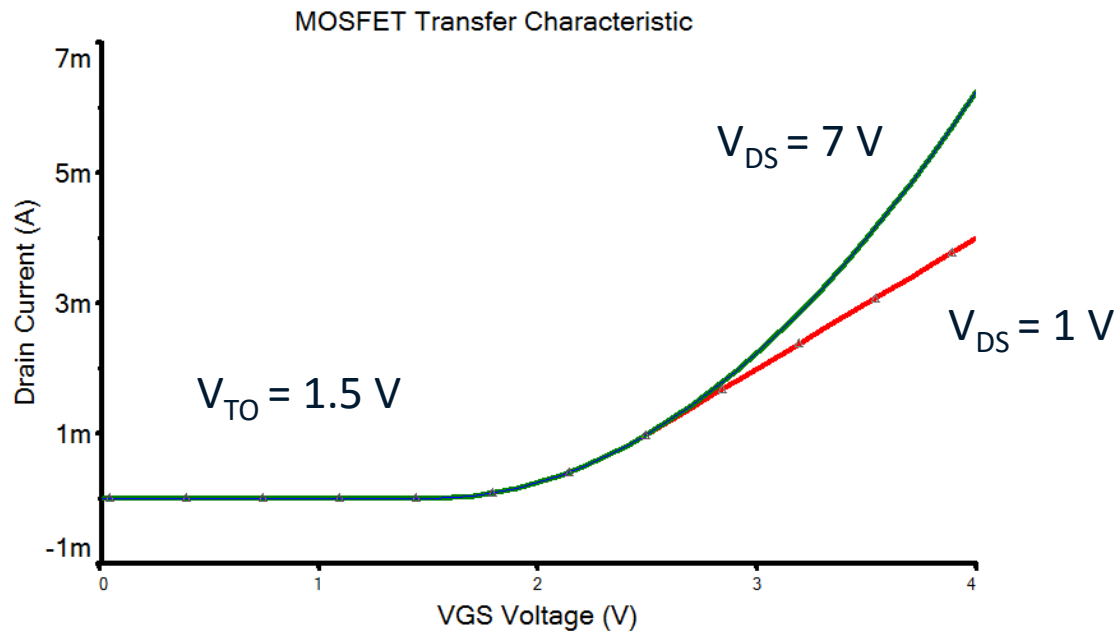

# Summary

- Introduced MOSFET characteristics
- Introduced dc biasing

# Next Lesson


- Common Source Amplifier: DC Analysis



**Dr. Allen Robinson**

Academic Professional  
School of Electrical and  
Computer Engineering

# Introduction to Electronics



*An introduction to electronic components and a study of circuits  
containing such devices.*





**Dr. Allen Robinson**  
Academic Professional  
School of Electrical and  
Computer Engineering

# Common Source Amplifier: DC Analysis

*Introduce common source amplifier*



# Previous Lesson


- Examined MOSFET characteristic curves and biasing

# Lesson Objectives


- Introduce common source amplifier
- Analyze common source amplifier dc circuit

# MOSFET Gain Stage

# Common Source Amplifier

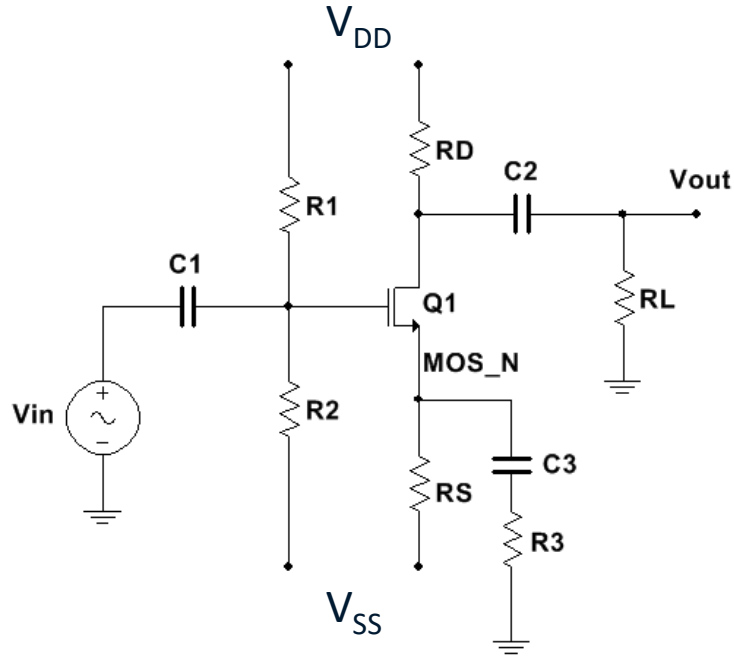


# Common Source Amplifier DC Circuit

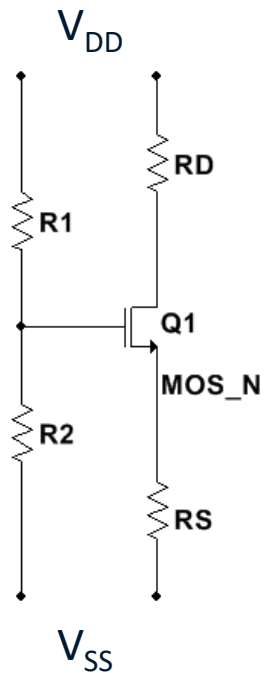

$$I_G = 0$$

$$I_D = I_S$$

# Common Source Amplifier DC Formulas

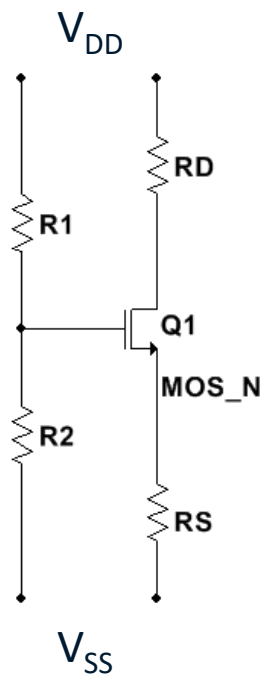

$$I_G = 0$$

$$I_D = I_S$$

$$V_G = \frac{V_{DD}R_2 + V_{SS}R_1}{R_1 + R_2}$$

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TO}$$

$$V_1 = V_G - V_{SS} - V_{TO}$$

$$I_D = \left( \frac{\sqrt{1 + 4KV_1R_S} - 1}{2\sqrt{K}R_S} \right)^2$$

$$V_D = V_{DD} - R_D I_D$$

$$V_S = V_{SS} + R_S I_S$$

# Summary

- Introduced common source (CS) amplifier
- Introduced dc analysis of CS amplifier



# Next Lesson


- Common Source Amplifier: AC Analysis



**Dr. Allen Robinson**

Academic Professional  
School of Electrical and  
Computer Engineering

# Introduction to Electronics



*An introduction to electronic components and a study of circuits  
containing such devices.*



**Dr. Allen Robinson**  
Academic Professional  
School of Electrical and  
Computer Engineering

# Common Source Amplifier: AC Analysis

*Examine ac behavior of the common source amplifier*



# Previous Lesson

- Introduced common source amplifier
- Introduced dc biasing

# Lesson Objectives

- Introduce ac behavior of CS amplifier
- Analyze CS amplifier circuit

# Small Signal Parameters and Gain


Perform small-signal analysis to obtain:

$$g_m = 2\sqrt{KI_D} \quad \text{Transconductance}$$


$$r_s = 1/g_m \quad \text{Intrinsic source resistance}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_D || R_L}{r_s + R_S || R_3} \quad \text{Midband Gain}$$

# Common Source Amplifier

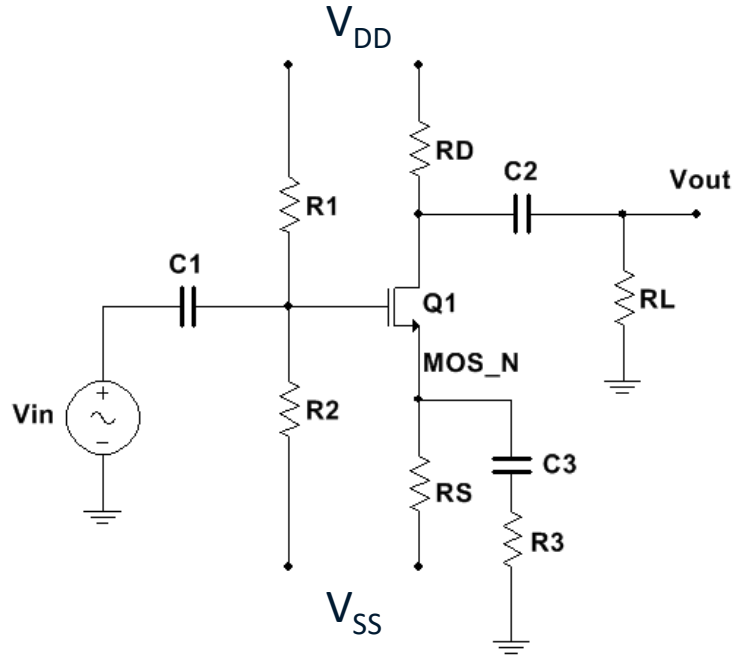

# Common Source Amplifier Example

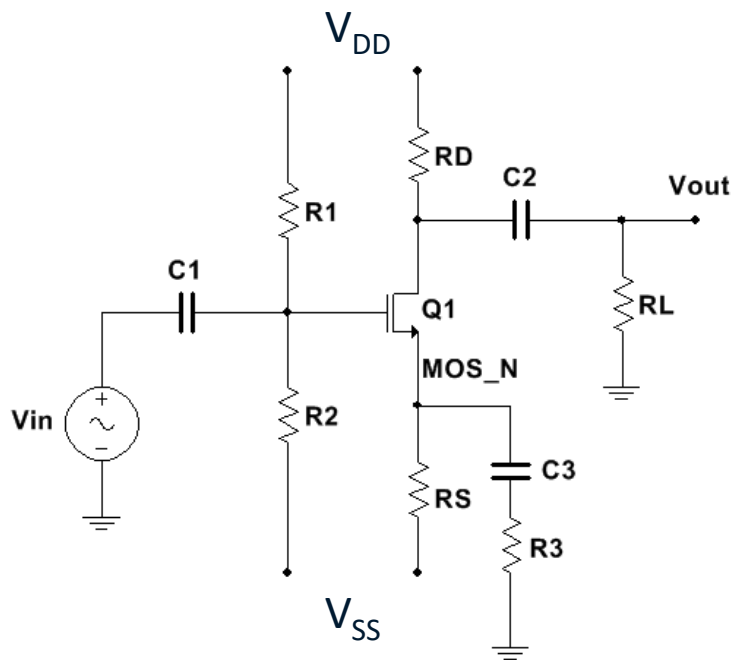

Determine Q point and Gain Given:

$$R_1 = 1 \text{ M}\Omega$$

$$V_{DD} = +15 \text{ V}$$

$$R_2 = 200 \text{ k}\Omega$$

$$V_{SS} = -15 \text{ V}$$

$$R_S = 3 \text{ k}\Omega$$

$$R_L = 20 \text{ k}\Omega$$

$$R_3 = 51 \Omega$$


$$R_D = 15 \text{ k}\Omega$$

$$K = 0.001 \text{ A/V}^2$$

$$V_{TO} = 1.5 \text{ V}$$



# Common Source Amplifier Example

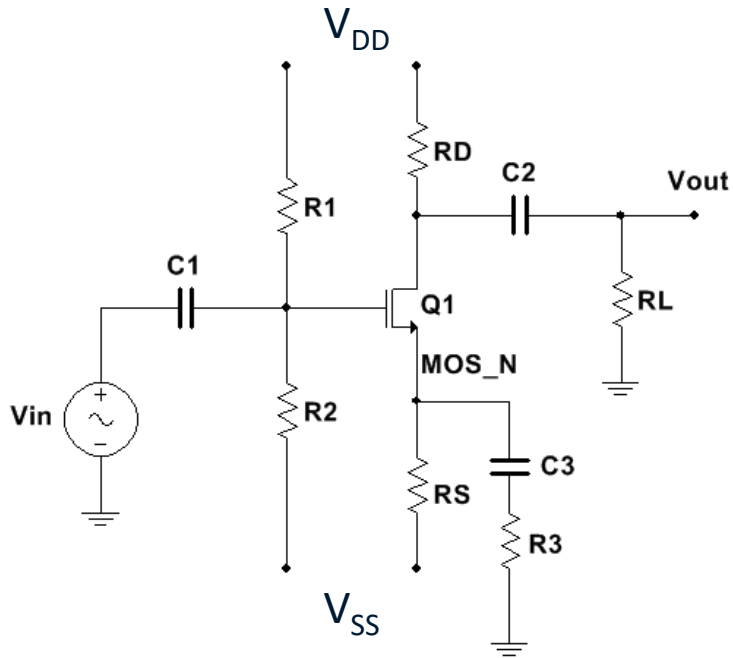

# Summary

- Introduced AC analysis of CS amplifier
- Analyzed CS amplifier circuit

# Next Lesson

- Bipolar Junction Transistor (BJT)